

Experiment-4 : Carry Look Ahead Adder

Objective:

To design a 4-bit carry look-ahead and test it using 4-bit up counter. The test bench should check the generated output with the expected output and prints pass/fail messages.

Tool Used:

Xilinx ISE.

Theory:

A regular CLA is implemented with 4 bits and the test pattern is generated in the test bench using always block and a local clock. The 2nd input is derived from the 1st counter input, carry is generated randomly.

DUT Code:

```
module cla(input [3:0]a, b, input cin, output [3:0]sum, output cout);
    wire [3:0]g,p;
    wire [4:1]x;

    assign g = a&b;
    assign p = a^b;

    assign sum = p^{x[3:1],cin};
    assign x[4:1] = g | (p & {x[3:1],cin});
    assign cout = x[4];
endmodule
```

TB Code:

```
module tb;
    reg [3:0] a,b; reg cin; reg clk = 0;
    wire [3:0] sum; wire cout;
    integer x = 0, y = 0;

    cla uut (a,b,cin,sum,cout);
    initial forever #5 clk = !clk;

    always@(posedge clk) begin
        a = y;
        b = y^1;
        cin = $random;
        y = y+1;
        #1;
    end
endmodule
```

```


        if((a+b+cin) != {cout,sum}) x = x+1;
    end

    initial begin
        #100;
        if(!x) $display("success");
        else $display("%d number of errors",x);
        $finish;
    end


endmodule

```

RTL Diagram:

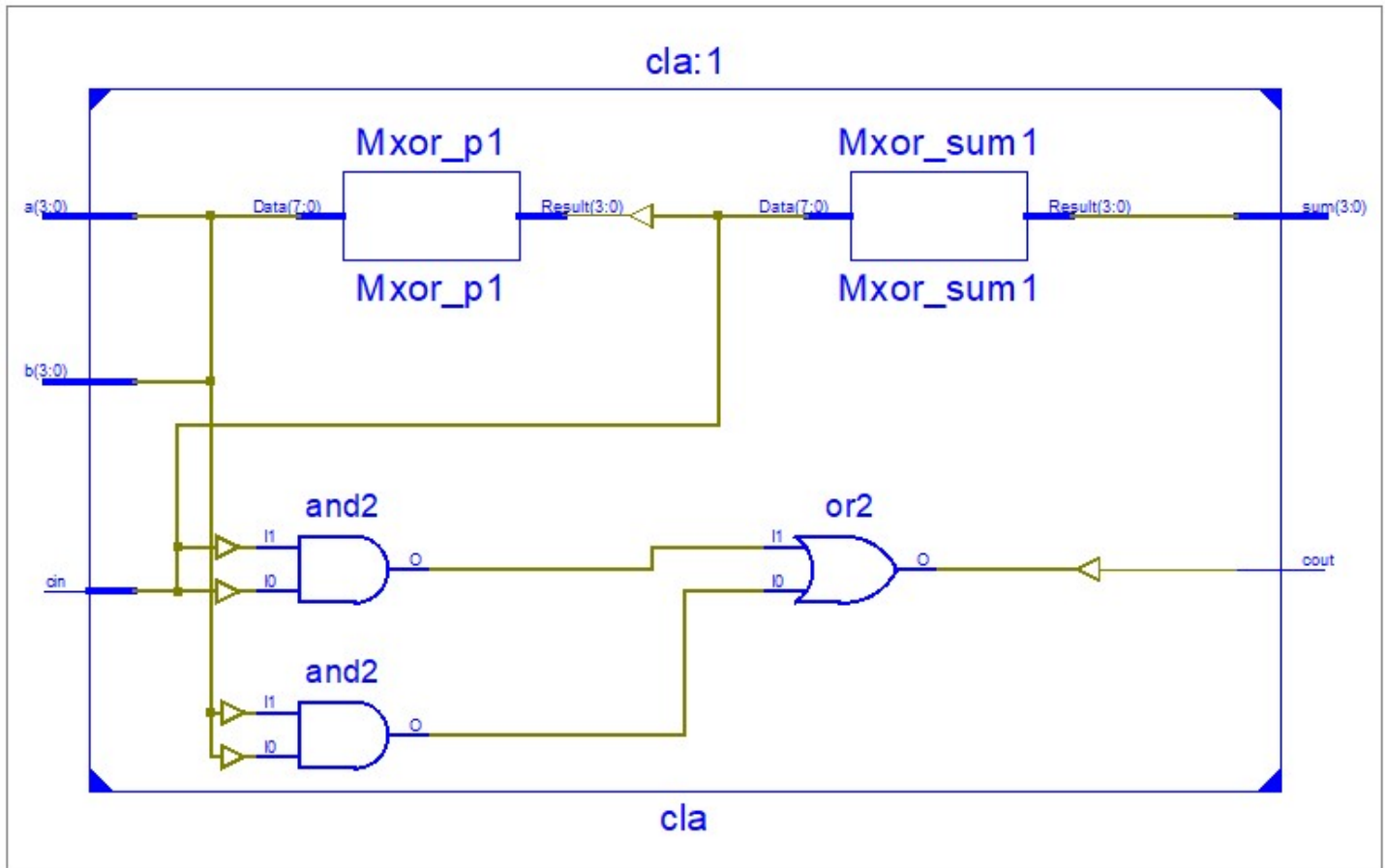

Output Waveform:

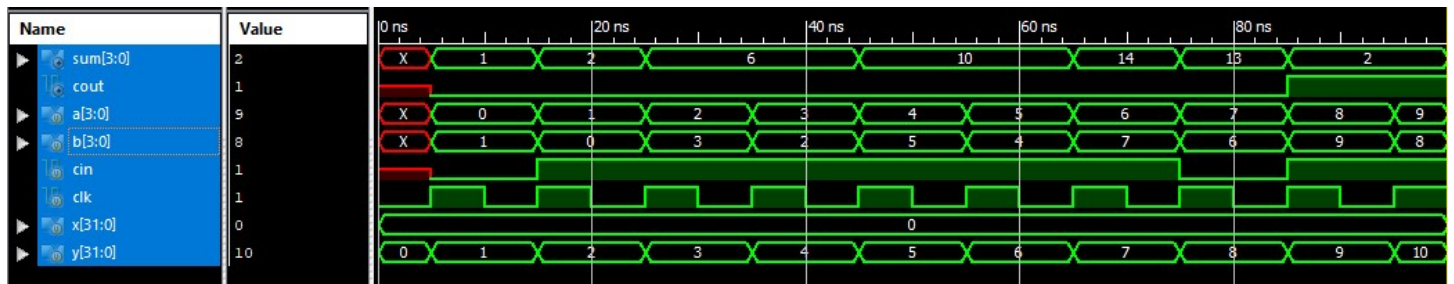

Simulation Output:

```
Console
ISim P.20131013 (signature 0x7708f090)
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
Success
---
```

Result:

The simulation output and the RTL diagram is observed and found to be valid.