

Experiment-1 : 4x1 Multiplexer

Objective:

To design a 4x1 Multiplexer and write a simple test bench for it. The test bench should generate stimulus to completely verify the functionality of the design under test with delay of 20ns.

Theory:

Multiplexer is a combinational circuit that has maximum of 2^n data inputs, 'n' selection lines and single output line. One of these data inputs will be connected to the output based on the values of selection lines such that, each combination will select only one data input.

DUT Code:


```
//Design
module mux(input [3:0]i, [1:0]s, output y);
    assign y = s[1]?(s[0]?i[3]:i[2]):(s[0]?i[1]:i[0]); //logic for mux
endmodule
```

TB Code:


```
//TB
module mux_tb;
    reg [3:0] i; // Input of mux
    reg [1:0] s; //select line of mux
    wire y; // output of mux
    integer x = 0; // integer to count error
    mux uut(i,s,y); //instantiation

    initial begin
        repeat(10)begin //test 10 times
            i = $random; // random input (4 bits)
            s = $random; // random select input (2 bits)
            #20; //20 ns delay as mentioned in exp requirement
            if (y != i[s]) x = x + 1; //check if y is mapped to correct input
        end
        if(!x) $display("Success"); //print success when no loop raises error
        else $display("Failure"); // else print failure
    end
endmodule
```

RTL Diagram:

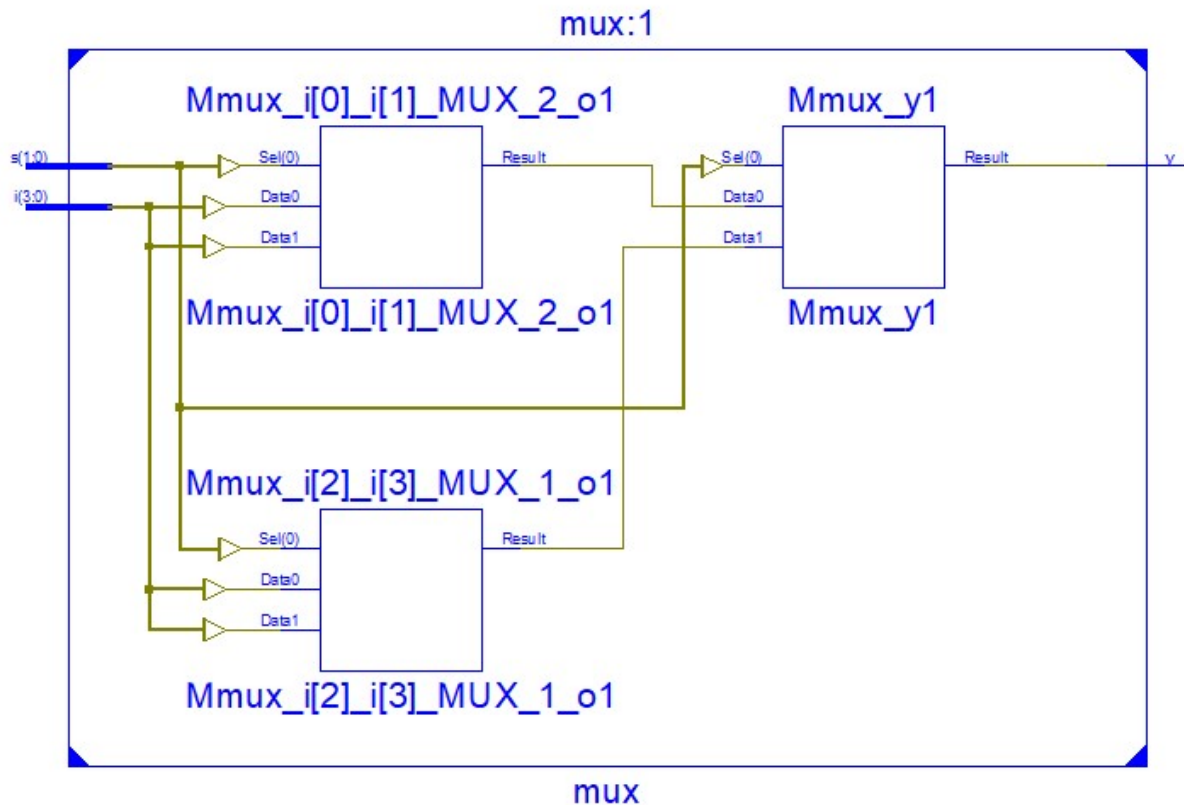

Output Waveform:

 

Simulation Output:

Console

ISim P.20131013 (signature 0x7708f090)
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
Success

Result:

The simulation output and the RTL diagram is observed and found to be valid.