

**DEPARTMENT OF ELECTRONICS & COMMUNICATION
ENGINEERING**



THAPAR INSTITUTE
OF ENGINEERING & TECHNOLOGY
(Deemed to be University)

**VLSI TESTING AND VERIFICATION
LAB FILE**


Submitted to,

**Dr. Gaganpreet Kaur
Asst. Professor**


Submitted by,

**T Raja Aadhithan
602162021
M.Tech (VLSI Design)**

RTL Diagram:

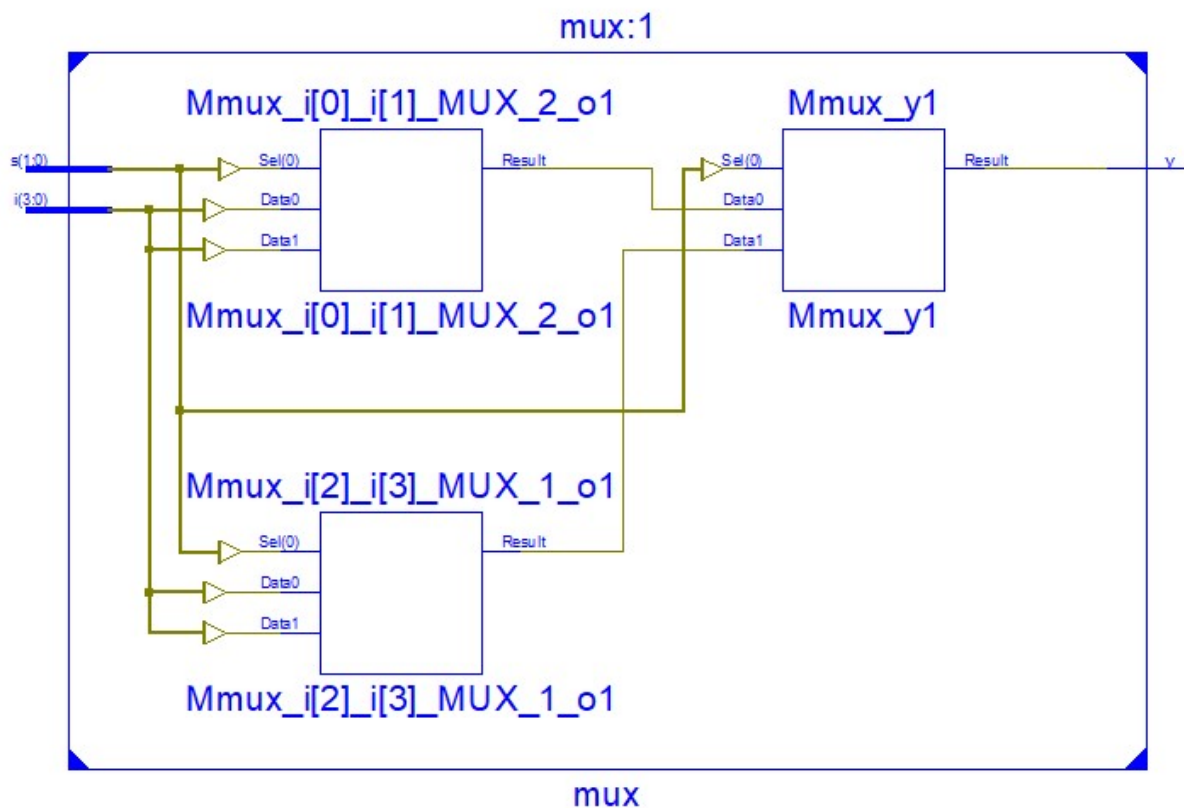

Output Waveform:

 

Simulation Output:

```

Console
-----
ISim P.20131013 (signature 0x7708f090)
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
Success
    
```

Experiment-1 : 4x1 Multiplexer

Objective:

To design a 4x1 Multiplexer and write a simple test bench for it. The test bench should generate stimulus to completely verify the functionality of the design under test with delay of 20ns.

Theory:

Multiplexer is a combinational circuit that has maximum of 2^n data inputs, 'n' selection lines and single output line. One of these data inputs will be connected to the output based on the values of selection lines such that, each combination will select only one data input.

DUT Code:

```
module mux(input [3:0]i, [1:0]s, output y);
    assign y = s[1]?(s[0]?i[3]:i[2]):(s[0]?i[1]:i[0]); //logic for mux
endmodule
```

TB Code:


```
module mux_tb;
    reg [3:0] i; // Input of mux
    reg [1:0] s; //select line of mux
    wire y; // output of mux
    integer x = 0; // integer to count error
    mux uut(i,s,y); //instantiation

    initial begin
        repeat(10)begin //test 10 times
            i = $random; // random input (4 bits)
            s = $random; // random select input (2 bits)
            #20; //20 ns delay as mentioned in exp requirement
            if (y != i[s]) x = x + 1; //check if y is mapped to correct input
        end
        if(!x) $display("Success"); //print success when no loop raises error
        else $display("Failure"); // else print failure
    end
endmodule
```

Result:

The simulation output and the RTL diagram is observed and found to be valid.

RTL Diagram:

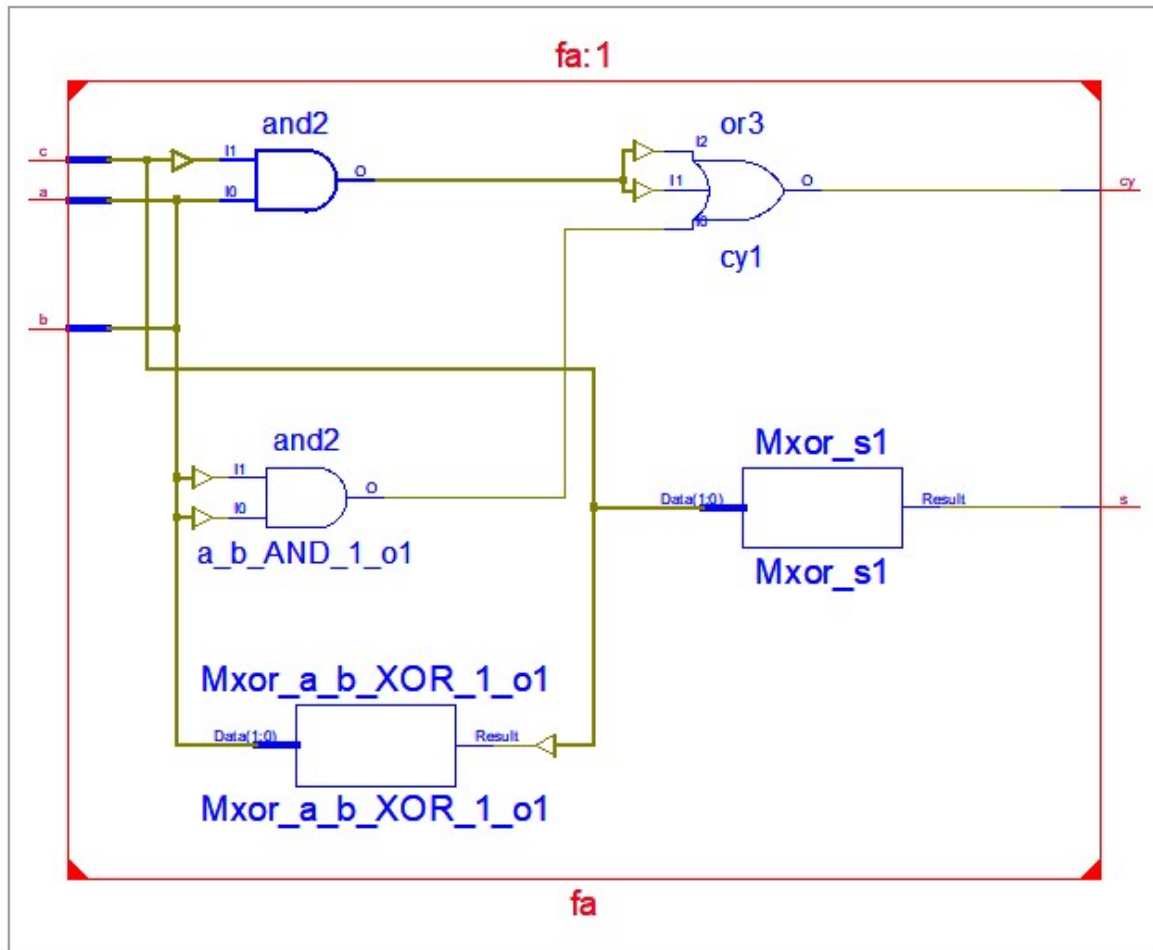

Output Waveform:



Simulation Output:

Console

ISim P.20131013 (signature 0x7708f090)
 This is a Full version of ISim.
 Time resolution is 1 ps
 Simulator is doing circuit initialization process.
 Finished circuit initialization process.
 SUCCESS

Experiment-2 : Full Adder

Objective:

To design a Single bit Full Adder and write a simple test bench for it. The test bench should generate stimulus to completely verify the functionality of the design.

Tool Used:

Xilinx ISE.

Theory:

In the case of Full Adder Circuit we have three inputs A, B and Carry In and we will get final output SUM and Carry out. So, $A + B + \text{CARRY IN} = \text{SUM}$ and CARRY OUT.

DUT Code:

```
module fa(input a,b,c, output s,cy);
    assign s = a^b^c; //logic for sum
    assign cy = a&b | b&c | a&c; //logic for carry
endmodule
```

TB Code:


```
module tb();
    reg a,b,c; //inputs
    wire s,cy; //outputs
    integer x=0; //error counter
    fa dut(a,b,c,s,cy); // instantiation

    initial begin
        repeat(100) begin //100 tests
            {a,b,c} = $random; //random input stimuli
            #1; //delay to see dut output
            if ({cy,s} != a+b+c) x = x+1; // check if the output is as expected
        end
        if(!x) $display("SUCCESS"); //print success if correct
        else $display("FAILURE"); //print failure is not
    end
endmodule
```


Result:

The simulation output and the RTL diagram is observed and found to be valid.

RTL Diagram:

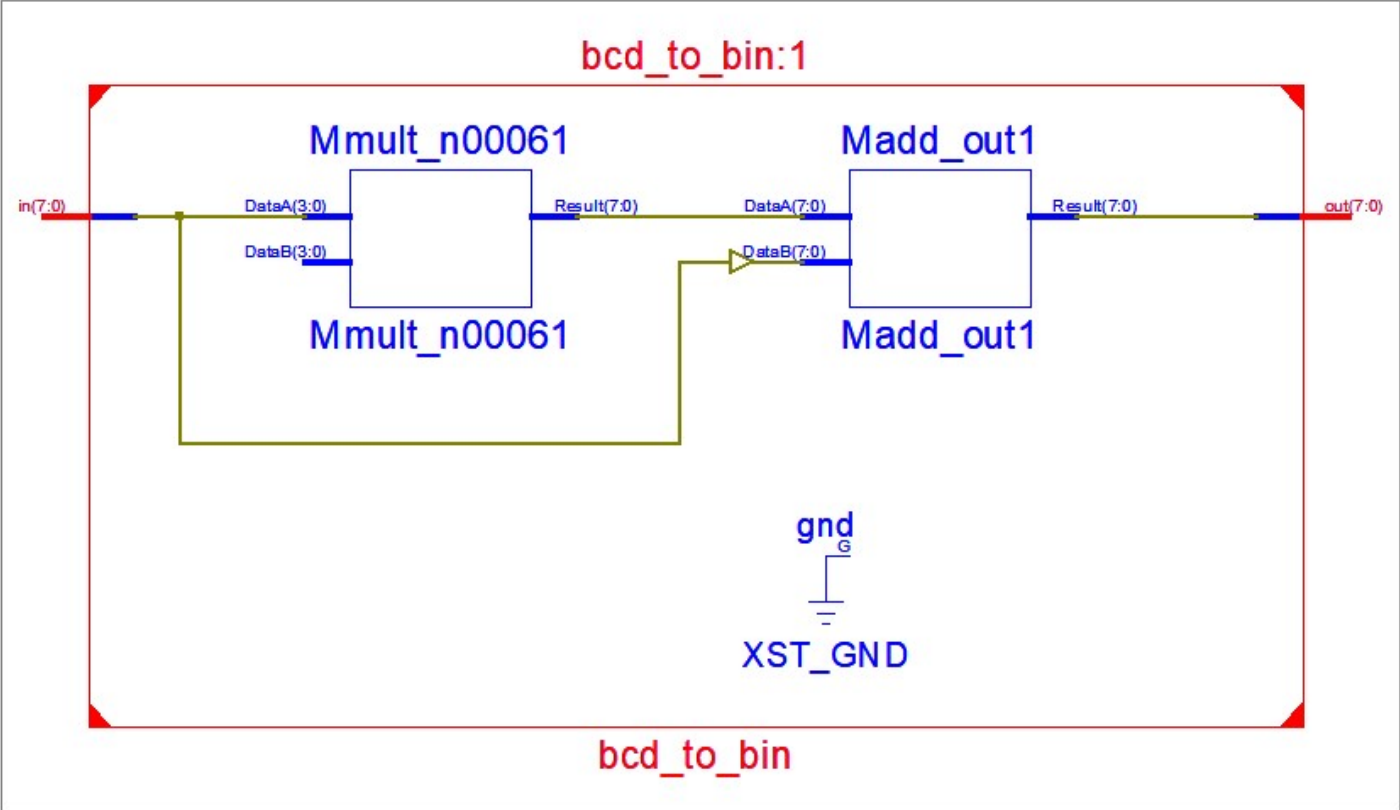

Output Waveform:

 

Simulation Output:

Console

ISim P.20131013 (signature 0x7708f090)
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
Success

Experiment-3 : BCD to Binary Converter

Objective:

To design a BCD to binary converter and write a simple test bench for it. The test bench should generate stimulus to completely verify the functionality of the design.

Tool Used:

Xilinx ISE.

Theory:

The value of 2^{nd} digit is multiplied with 10 and added to the lower bit.

DUT Code:

```
module bcd_to_bin(input [7:0]in, output [7:0]out);
    assign out = in[7:4]*10 + in[3:0]; //logic for conversion
endmodule
```

TB Code:

```
module tb();
    reg [7:0]in; wire [7:0] out;
    integer x=0;
    reg [3:0] y;
    bcd_to_bin dut(in,out);


    initial begin
        repeat(10)begin
            y = $random; //generating random input
            if (y > 9) y = y+6; //restricting it between 0 and 9
            in[3:0] = y; //assigning it to the lower bit

            y = $random; //generating random input
            if (y > 9) y = y+6; //restricting it between 0 and 9
            in[7:4] = y; //assigning it to the upper bit
            #1;
            if(out != in[7:4]*10 + in[3:0]) x = x+1; // self check if it is same
        end
        if(!x) $display("Success"); //print success when no loop raises error
        else $display("Failure"); // else print failure
    end
endmodule
```

Result:

The simulation output and the RTL diagram is observed and found to be valid.

RTL Diagram:

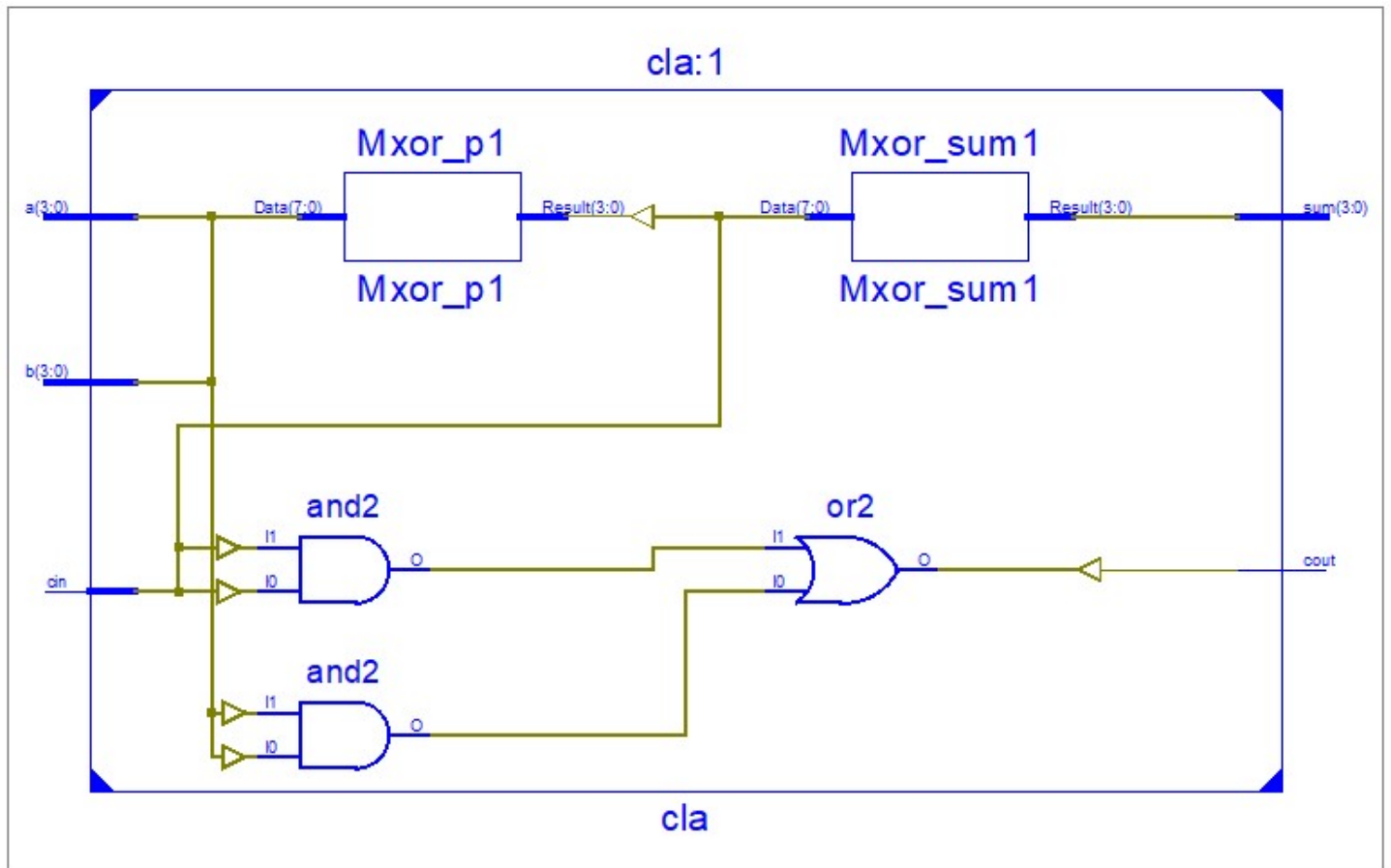

Experiment-4 : Carry Look Ahead Adder

Objective:

To design a 4-bit carry look-ahead and test it using 4-bit up counter. The test bench should check the generated output with the expected output and prints pass/fail messages.

Tool Used:

Xilinx ISE.

Theory:

A regular CLA is implemented with 4 bits and the test pattern is generated in the test bench using always block and a local clock. The 2nd input is derived from the 1st counter input, carry is generated randomly.

DUT Code:

```
module cla(input [3:0]a, b, input cin, output [3:0]sum, output cout);
    wire [3:0]g,p;
    wire [4:1]x;

    assign g = a&b;
    assign p = a^b;

    assign sum = p^{x[3:1],cin};
    assign x[4:1] = g | (p & {x[3:1],cin});
    assign cout = x[4];
endmodule
```


TB Code:

```
module tb;
    reg [3:0] a,b; reg cin; reg clk = 0;
    wire [3:0] sum; wire cout;
    integer x = 0, y = 0;

    cla uut (a,b,cin,sum,cout);
    initial forever #5 clk = !clk;

    always@(posedge clk) begin
        a = y;
        b = y^1;
        cin = $random;
        y = y+1;
        #1;
    end
endmodule
```

Output Waveform:

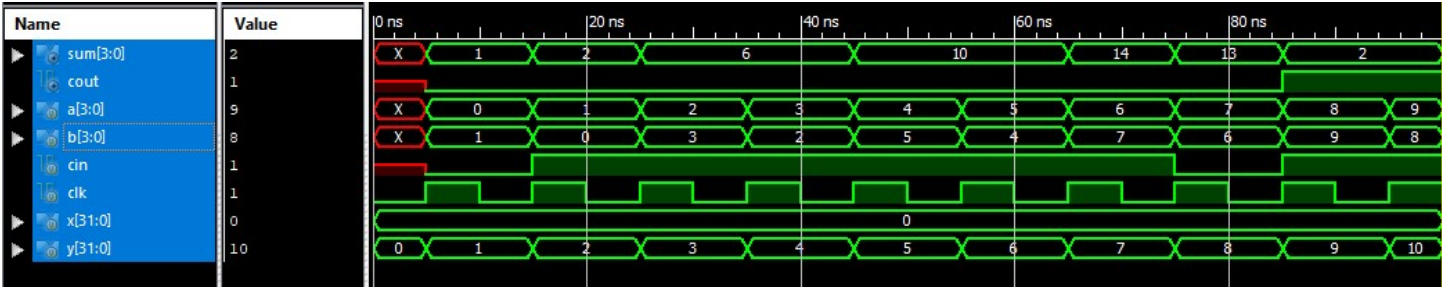

Simulation Output:

```
Console
ISim P.20131013 (signature 0x7708f090)
This is a Full version of ISim.
Time resolution is 1 ps
Simulator is doing circuit initialization process.
Finished circuit initialization process.
Success
```

```
        if((a+b+cin) != {cout,sum}) x = x+1;
    end


    initial begin
        #100;
        if(!x) $display("success");
        else $display("%d number of errors",x);
        $finish;
    end

endmodule
```

Result:

The simulation output and the RTL diagram is observed and found to be valid.

RTL Diagram:

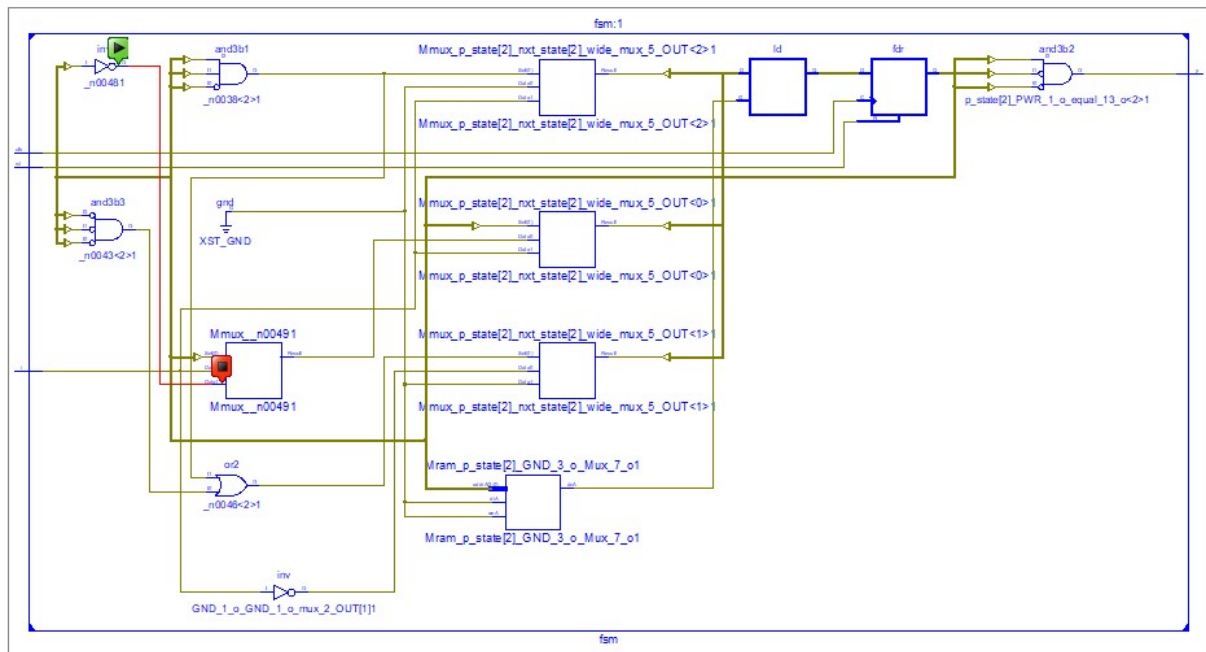

Experiment-5 : Sequence Detector

Objective:

To design a Moore FSM that detects the sequence 1001. The test bench should check the generated output with the expected output and prints pass/fail messages.

Tool Used:

Xilinx ISE.

Theory:

A FSM detects the matching of input sequence and triggers the output, a self checking test bench is stimulated using shift registers as 4 bit memory and the output is verified.

DUT Code:

```
module fsm(input i,rst,clk, output y);
    parameter idle=3'b000, s1=3'b001, s10=3'b010, s100=3'b011, s1001=3'b100;
    reg [2:0] p_state,nxt_state;

    always@(*)begin
        case(p_state)
            idle      : nxt_state <= i ? s1      : idle;
            s1        : nxt_state <= i ? s1      : s10    ;
            s10       : nxt_state <= i ? s1      : s100;
            s100      : nxt_state <= i ? s1001: idle;
            s1001     : nxt_state <= i ? s1      : s10    ;
        endcase
    end

    always@(posedge clk)begin
        if(rst) p_state <= idle;
        else p_state <= nxt_state;
    end

    assign y = (p_state == s1001) ? 1 : 0;
endmodule
```

TB Code:


```
module tb;

    reg i=0,rst,clk=0;// Inputs
    wire y;// Output
    fsm uut (i,rst,clk,y);// Instantiate the Unit Under Test (UUT)
    reg [3:0]q=0    ;
    integer err = 0;

    initial forever #5 clk = !clk;
    initial forever @(posedge clk) q <= {q[2:0],i};

    initial begin
        $monitor("%0d : input i = %b state is %d, output y = %b ",$time,i,uut.p_state,y);
    end
endmodule
```

Output Waveform:

 

Simulation Output:

```

0 : input i = 0 state is x, output y = x
5 : input i = 0 state is 0, output y = 0
10 : input i = 1 state is 0, output y = 0
15 : input i = 1 state is 1, output y = 0
20 : input i = 0 state is 1, output y = 0
25 : input i = 0 state is 2, output y = 0
35 : input i = 0 state is 3, output y = 0
40 : input i = 1 state is 3, output y = 0
45 : input i = 1 state is 4, output y = 1
50 : input i = 0 state is 4, output y = 1
55 : input i = 0 state is 2, output y = 0
65 : input i = 0 state is 3, output y = 0
70 : input i = 1 state is 3, output y = 0
75 : input i = 1 state is 4, output y = 1
80 : input i = 0 state is 4, output y = 1
85 : input i = 0 state is 2, output y = 0
90 : input i = 1 state is 2, output y = 0
95 : input i = 1 state is 1, output y = 0
100 : input i = 0 state is 1, output y = 0
105 : input i = 0 state is 2, output y = 0
115 : input i = 0 state is 3, output y = 0
125 : input i = 0 state is 0, output y = 0
130 : input i = 1 state is 0, output y = 0
135 : input i = 1 state is 1, output y = 0
140 : input i = 0 state is 1, output y = 0
145 : input i = 0 state is 2, output y = 0
155 : input i = 0 state is 3, output y = 0
160 : input i = 1 state is 3, output y = 0
165 : input i = 1 state is 4, output y = 1
175 : input i = 1 state is 1, output y = 0
success

```

```

rst = 1'b1;
#10;
rst = 1'b0;
@(negedge clk) i = 1;
@(negedge clk) i = 0;
@(negedge clk) i = 0;
@(negedge clk) i = 1;
@(negedge clk) i = 0;
@(negedge clk) i = 0;
@(negedge clk) i = 1;
@(negedge clk) i = 0;
@(negedge clk) i = 1;
@(negedge clk) i = 0;
@(negedge clk) i = 0;
@(negedge clk) i = 0;
@(negedge clk) i = 1;
@(negedge clk) i = 0;
@(negedge clk) i = 0;
@(negedge clk) i = 1;
#100;
if(err) $display("error"); else $display("success");
#20;
$finish;
end

always@(q)begin
    if(q == 4'b1001)begin
        @(negedge clk);
        if(!y) err = err+1;
    end
end


endmodule

```


Result:

The simulation output and the RTL diagram is observed and found to be valid.

RTL Diagram:

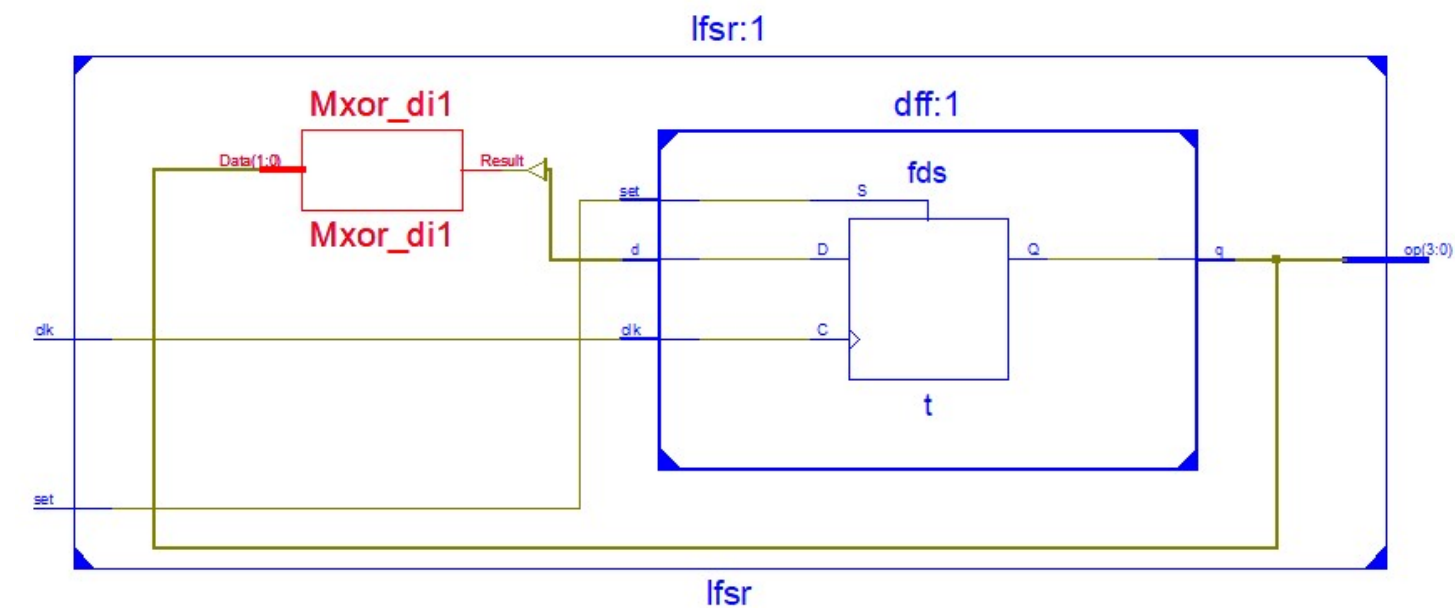

Output Waveform:

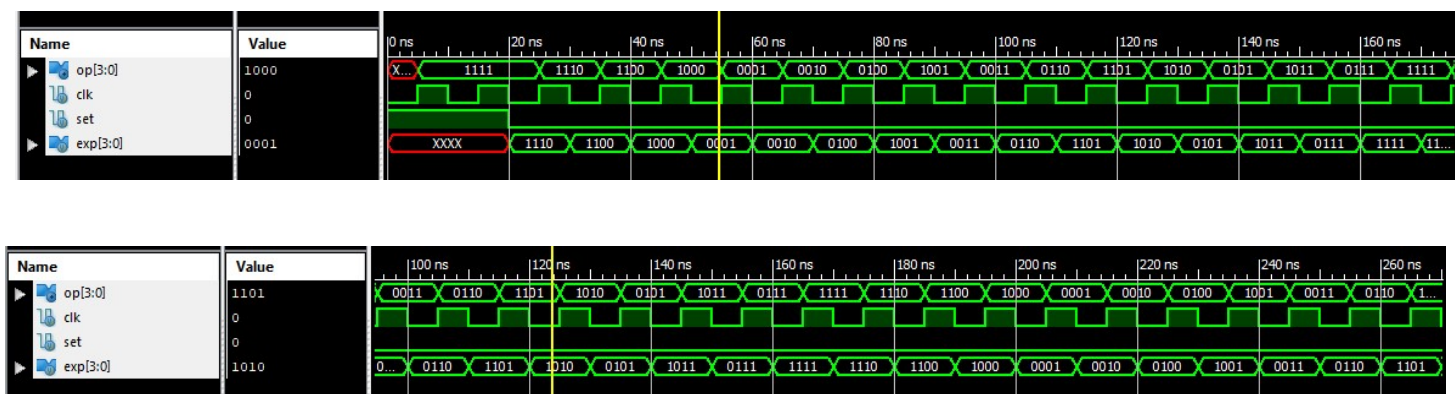

Experiment-6 : 4 bit LFSR

Objective:

To design a 4 bit LFSR with characteristic polynomial $1+x^3+x^4$ and to write a self checking test bench for it.

Tool Used:

Xilinx ISE.

Theory:

LFSR generates pseudo random output of size 2^n-1 . The output of register corresponding to the polynomial is XOR'd and fed into the input.

DUT Code:

```
module dff(input d,clk,set,output q);
    reg t;
    always@(posedge clk) begin
        if(set) t<=1'b1;
        else t <= d;
    end
    assign q = t;
endmodule

module lfsr(input clk,set,output [3:0]op);
    wire di;
    wire [3:0]q;
    assign di = q[3]^q[2];
    dff f1(di,clk,set,q[0]);
    dff f2(q[0],clk,set,q[1]);
    dff f3(q[1],clk,set,q[2]);
    dff f4(q[2],clk,set,q[3]);
    assign op = q;
endmodule
```

TB Code:

```
module tb;
    reg clk=0;
    reg set;
    reg [3:0]exp;
    wire [3:0]op;
    lfsr uut (clk,set,op);

    initial forever #5 clk = !clk;
```

Simulation Output:

Finished circuit initialization process.

failure

success

success

success

success

success

success

success

success

success

success

success

success

success

success

success

success

success

success

success

success

```
initial begin
    set = 1;
    #20 set = 0;
    repeat(30)begin
        @(negedge clk);
        if(uut.q == exp) $display("success");
        else $display("failure");
        exp = uut.q;
        exp = {exp[2:0],exp[3]^exp[2]};
    end
end
endmodule
```

Result:

The simulation output and the RTL diagram is observed and found to be valid.